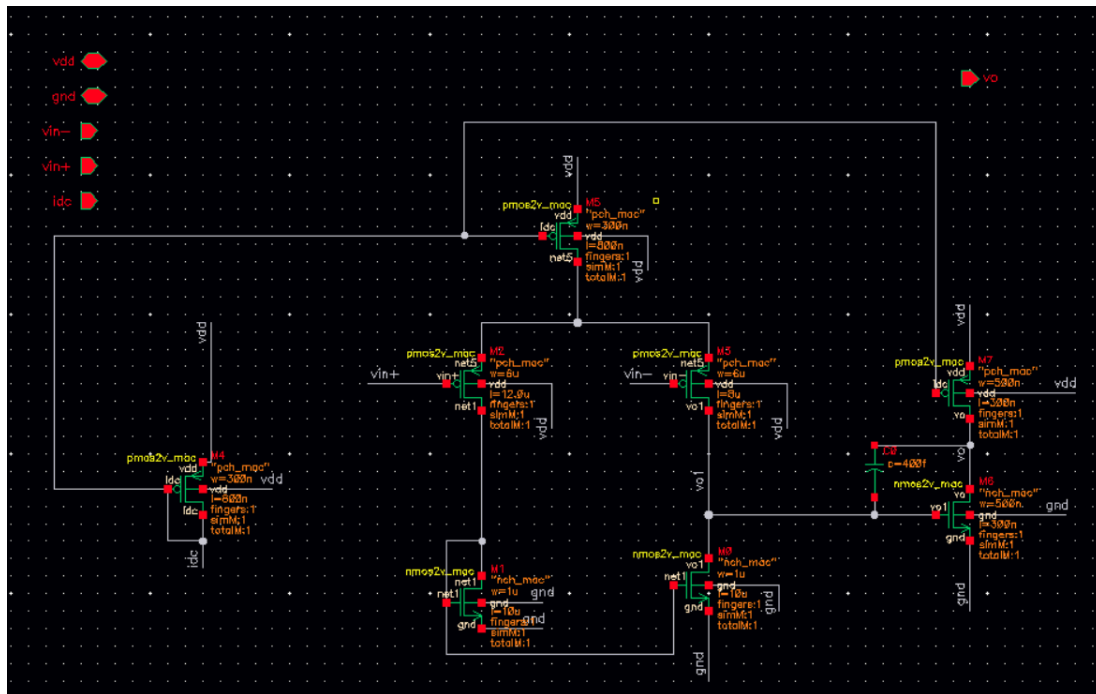


2-Stage Miller Compensated opamp

Specifications :

- Input common-mode voltage : 250mV
- Minimum supply voltage : 1.6V
- Temperature Range : -40oC to 125oC
- Open loop-gain : > 75dB
- Load capacitance : 1pF
- Unity gain frequency : > 1MHz
- Power consumption : < 10uW
- Phase margin : atleast 60 deg (considering worst cases)

Schematic:



A current mirror is used to maintain stability across PVT variations. It ensures the set reference current flows through the transistors. It eliminates the need for multiple current sources.

II. Differential Amplifier:

1. PMOS differential input pair:

Since input common mode voltage is small(around 250mV), PMOS is preferred since it doesn't need that high a voltage to turn ON.

2. NMOS active load pair:

NMOS allows the same current with a smaller overdrive voltage leaving more room for output swing.

III. CS Amplifier:

Vout from differential amplifier is reasonably high so we feed it into the gate of an NMOS transistor for further amplification. NMOS transistors also have a higher g_m in general so we can get achieve a higher gain.

IV. Miller compensation

Adding a miller capacitor introduces a dominant pole in the frequency response ensuring sufficient phase margin(reducing phase shift at unity gain frequency).

Design Procedure :

Power: < 10uW

max vdd=1.98(considering 10% variation)

⇒ total current < 5.05uA

total current = current through differential amp + current through cs amp + I_{ref}

$I_{ref} = 700n$

current through differential amp = 700n(divided both ways)

current through cs amp = 2.8u (trying to let max possible current for high g_m)

Unity gain bandwidth: > 1MHz

$$w_u = \frac{gm_1}{Cc} > > 10^6$$

$$gm_1 > > 400 \cdot 10^{-15} \cdot 10^6$$

$$gm_1 = 400 \cdot 10^{-15} \cdot 10^6 \cdot 10 = 4u$$

Phase margin: atleast 60 degrees

$$180 - \tan^{-1}(gm_1 r_1 r_2 gm_2) - \tan^{-1}\left(\frac{gm_1}{gm_2} \cdot \frac{1pF}{Cc}\right) - \tan^{-1}\left(\frac{gm_1}{gm_2}\right)$$

$$90 - \tan^{-1}\left(\frac{gm_1}{gm_2} \cdot \frac{1pF}{Cc}\right) - \tan^{-1}\left(\frac{gm_1}{gm_2}\right)$$

$$\tan^{-1}\left(\frac{gm_1}{gm_2} \cdot \frac{1pF}{Cc}\right) + \tan^{-1}\left(\frac{gm_1}{gm_2}\right) < 30$$

$$\tan^{-1}\left(\frac{gm_1}{gm_2} \cdot \frac{1pF}{Cc}\right) < < 30$$

$$\frac{4 \cdot 10^{-6}}{\tan(30)} \cdot \frac{10^{-12}}{800 \cdot 10^{-15}} < < gm_2$$

$$gm_2 > > 8.6u$$

Gain : >75dB (open loop)

$$A = gm_1 \cdot gm_2 \cdot r_1 \cdot r_2$$

$$r_1 = r_{o3} \parallel r_{o0}$$

$$r_2 = r_{o7} \parallel r_{o6}$$

gm1	4.179u
ron1	180.3M
rop1	124.2M
gm2	34.59u
ro1	657.6K
ro2	3.799M
r1	73.54M
r2	560.6K
gain	5.959K
gain_db	75.5

by fixing the ratio (w/L), the value of ro can be increased by increasing magnitude of w and L thereby effectively increasing gain

Sizing :

1. M4, M5 have the same size(current mirror)

$$\left(\frac{w}{L} \right) = \frac{I_D}{UnCox \cdot (V_{GS} - V_{TH})^2} = \frac{700n}{(177 \cdot 10^{-6}) \cdot (0.1)^2}$$

(w/L)=0.39

Vov is set to 100mV to account for PVT variations and square law is used to approximate values

2. M7 needs to provide a current that is 4 times higher(CS Amp) so (w/L is 0.39*4=1.56)

had to use a slightly higher value(1.66) to meet the current requirements

3. PMOS differential pair(set gm so that ugb>1MHz)

$$gm_1 = 400 \cdot 10^{-15} \cdot 10^6 \cdot 10 = 4u$$

$$gm = 2 \cdot \frac{I_D}{(V_{ov})}$$

$$V_{ov} = \left(\frac{(4 \cdot 10^{-6})}{2 \cdot 350 \cdot 10^{-9}} \right)^{-1} = 175m$$

$$\left(\frac{w}{L} \right) = \frac{gm}{UnCox(V_{ov})} = \frac{(4 \cdot 10^{(-6)})}{(177 \cdot 10^{-6}) \cdot (0.175)} = 0.13$$

since square law is only an approximation I used the following eqn to adjust v_{ov} and get the required g_m

$$V_{GS} = V_{TH} + \sqrt{\frac{2I_D}{\mu_n C_{ox} \left(\frac{w}{L}\right)}}$$

4. NMOS Active Load

only requirement is to bias it such that its in saturation
current will be 350n

$$\left(\frac{w}{L}\right) = \frac{I_D}{\mu_n C_{ox} \cdot (V_{GS} - V_{TH})^2} = \frac{350n}{(495.3 \cdot 10^{-6}) \cdot (0.2)^2} = 0.07$$

had to use $w/L = 0.1$

5. NMOS (cs amp)


$g_{m2} = 40\mu$ (10 times g_{m1} for good phase margin)

$$g_m = 2 \cdot \frac{I_D}{(V_{ov})}$$


$$V_{ov} = \left(\frac{40 \cdot 10^{-6}}{2 \cdot 2.8 \cdot 10^{-6}} \right)^{-1} = 140m$$

$$\left(\frac{w}{L}\right) = \frac{g_m}{\mu_n C_{ox} (V_{ov})} = \frac{(40 \cdot 10^{-6})}{(177.3 \cdot 10^{-6}) \cdot (0.14)} = 1.6$$

Test setup :

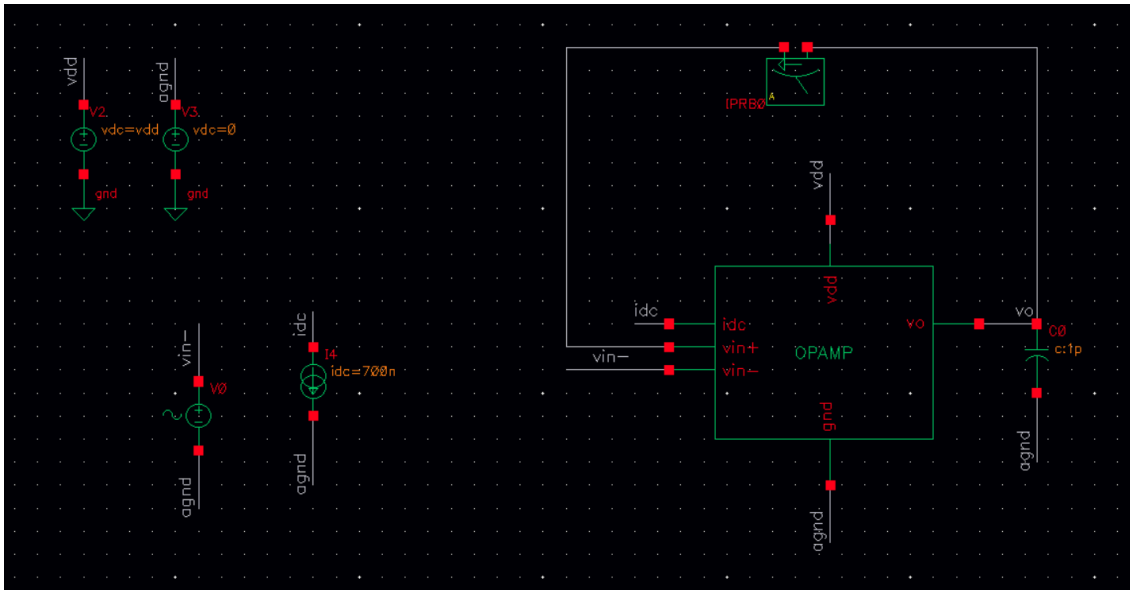


DC Operating Point :

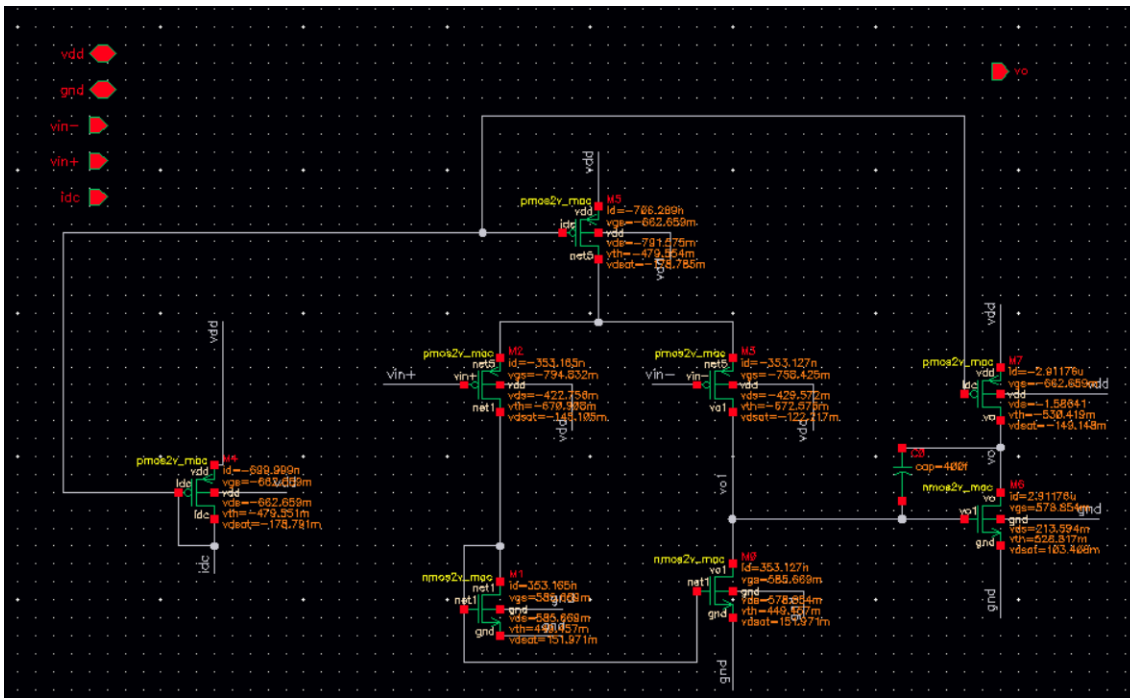

ADE Setup :

vdd → 1.62 1.8 1.98

id1	expr	(- OP("/I0/M3" "ids"))
id2	expr	(- OP("/I0/M7" "ids"))
power	expr	((id1 + id2 + 7e-07) * VAR("vdd"))


Choosing Analyses -- ADE Assembler@eecs-ser2.iiit.ac.in
✕

Analysis

<input type="radio"/> tran	<input type="radio"/> dc	<input type="radio"/> ac	<input type="radio"/> noise
<input type="radio"/> xf	<input type="radio"/> sens	<input type="radio"/> dcmatch	<input type="radio"/> acmatch
<input checked="" type="radio"/> stb	<input type="radio"/> pz	<input type="radio"/> lf	<input type="radio"/> sp
<input type="radio"/> envlp	<input type="radio"/> pss	<input type="radio"/> pac	<input type="radio"/> pstb
<input type="radio"/> pnoise	<input type="radio"/> pxf	<input type="radio"/> psp	<input type="radio"/> qpss
<input type="radio"/> qpac	<input type="radio"/> qpnoise	<input type="radio"/> qpxf	<input type="radio"/> qpss
<input type="radio"/> hb	<input type="radio"/> hbac	<input type="radio"/> hbstb	<input type="radio"/> hbnoise
<input type="radio"/> hbsp	<input type="radio"/> hbxf		

Stability Analysis

Sweep Variable

☒ Frequency

☐ Design Variable

☐ Temperature

☐ Component Parameter

☐ Model Parameter

☐ None

Sweep Range


☒ Start-Stop Start Stop

☐ Center-Span

Sweep Type

☒ Points Per Decade

☐ Number of Steps

Logarithmic 

Add Specific Points ☐

Add Points By File ☐


Probe Instance/Terminal

Local Ground Name

Enabled ☒

Corners	<input checked="" type="checkbox"/> Nominal	<input type="checkbox"/> tt	<input type="checkbox"/> ss	<input type="checkbox"/> ff
Temperature		-40 27 125	-40 27 125	-40 27 125
Design Variables				
Click to add				
Parameters				
Click to add				
Model Files				
cor_std_mos.scs		<input checked="" type="checkbox"/> tt	<input checked="" type="checkbox"/> ss	<input checked="" type="checkbox"/> ff
cr018gpil_v1d0.scs		<input checked="" type="checkbox"/> stat_noise	<input checked="" type="checkbox"/> stat_noise	<input checked="" type="checkbox"/> stat_noise
Click to add				
Model Group(s)		<modelgroup>	<modelgroup>	<modelgroup>
Click to add				
Tests				
<input checked="" type="checkbox"/> ..._opamp_tb_1	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
<input type="checkbox"/> ..._opamp_tb_2	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
<input type="checkbox"/> ..._opamp_tb_3	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
...mber of Corners	1	3	3	3

Results :

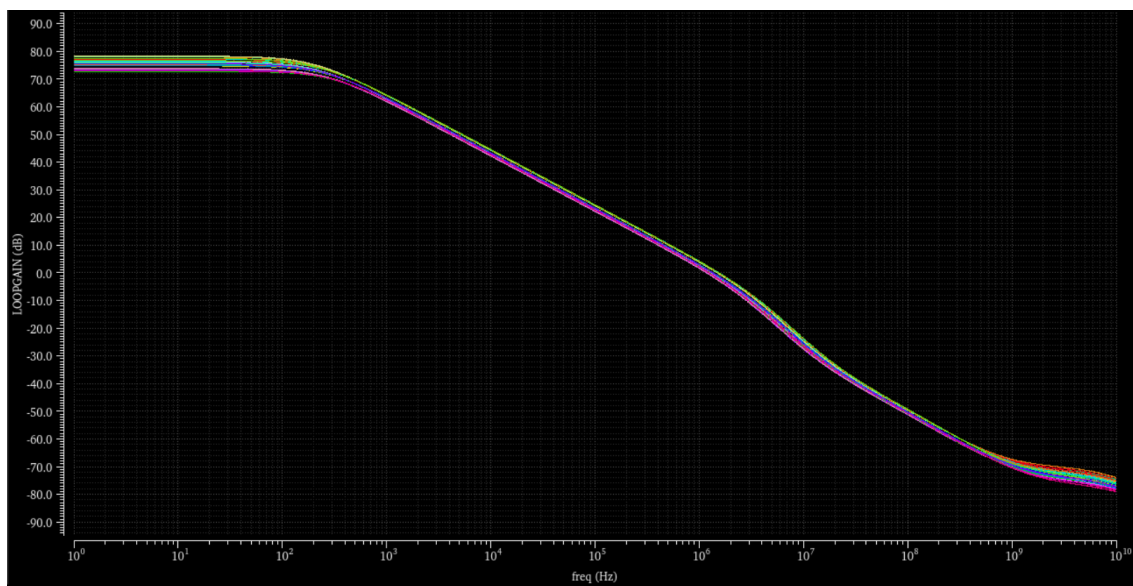

42 rows													
Point	Output	Nominal	Pass/Fail	tt_0	tt_1	tt_2	ss_0	ss_1	ss_2	ff_0	ff_1	ff_2	
Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter
Parameters: vdd=1.62													
1	/vo												
1	ro2	2	pass	2	2	2	2	2	2	2	2	2	2
1	OP[*/IO/M6* "re...	2	pass	2	2	2	2	2	2	2	2	2	2
1	OP[*/IO/M5* "re...	2	pass	2	2	2	2	2	2	2	2	2	2
1	OP[*/IO/M4* "re...	2	pass	2	2	2	2	2	2	2	2	2	2
1	OP[*/IO/M3* "re...	2	pass	2	2	2	2	2	2	2	2	2	2
1	OP[*/IO/M2* "re...	2	pass	2	2	2	2	2	2	2	2	2	2
1	OP[*/IO/M1* "re...	2	pass	2	2	2	2	2	2	2	2	2	2
1	OP[*/IO/M0* "re...	2	pass	2	2	2	2	2	2	2	2	2	2
1	Phase Margin	60.23		59.27	60.23	59.98	57.52	58.77	58.86	60.42	61.26	60.8	
1	Phase Margin Fr...	1.325M		1.506M	1.325M	1.209M	1.478M	1.295M	1.178M	1.533M	1.355M	1.241M	
1	Loop Gain Phase												
1	Loop Gain dB20												
1	power	6.345u		5.844u	6.345u	6.809u	5.482u	5.994u	6.51u	6.078u	6.558u	6.967u	
Parameters: vdd=1.8													
2	/vo												
2	ro2	2	pass	2	2	2	2	2	2	2	2	2	2
2	OP[*/IO/M6* "re...	2	pass	2	2	2	2	2	2	2	2	2	2
2	OP[*/IO/M5* "re...	2	pass	2	2	2	2	2	2	2	2	2	2
2	OP[*/IO/M4* "re...	2	pass	2	2	2	2	2	2	2	2	2	2
2	OP[*/IO/M3* "re...	2	pass	2	2	2	2	2	2	2	2	2	2
2	OP[*/IO/M2* "re...	2	pass	2	2	2	2	2	2	2	2	2	2
2	OP[*/IO/M1* "re...	2	pass	2	2	2	2	2	2	2	2	2	2
2	OP[*/IO/M0* "re...	2	pass	2	2	2	2	2	2	2	2	2	2
2	Phase Margin	60.62		59.6	60.62	60.43	57.84	59.15	59.32	60.77	61.65	61.25	
2	Phase Margin Fr...	1.326M		1.513M	1.326M	1.208M	1.485M	1.297M	1.176M	1.54M	1.356M	1.24M	
2	Loop Gain Phase												
2	Loop Gain dB20												
2	power	7.137u		6.576u	7.137u	7.655u	6.158u	6.732u	7.309u	6.853u	7.388u	7.843u	
Parameters: vdd=1.98													
3	/vo												
3	ro2	2	pass	2	2	2	2	2	2	2	2	2	2
3	OP[*/IO/M6* "re...	2	pass	2	2	2	2	2	2	2	2	2	2
3	OP[*/IO/M5* "re...	2	pass	2	2	2	2	2	2	2	2	2	2
3	OP[*/IO/M4* "re...	2	pass	2	2	2	2	2	2	2	2	2	2
3	OP[*/IO/M3* "re...	2	pass	2	2	2	2	2	2	2	2	2	2
3	OP[*/IO/M2* "re...	2	pass	2	2	2	2	2	2	2	2	2	2
3	OP[*/IO/M1* "re...	2	pass	2	2	2	2	2	2	2	2	2	2
3	OP[*/IO/M0* "re...	2	pass	2	2	2	2	2	2	2	2	2	2
3	Phase Margin	60.95		59.92	60.95	60.82	58.15	59.49	59.72	61.09	62.01	61.65	
3	Phase Margin Fr...	1.327M		1.519M	1.327M	1.206M	1.49M	1.298M	1.175M	1.546M	1.357M	1.238M	
3	Loop Gain Phase												
3	Loop Gain dB20												
3	power	7.941u		7.321u	7.941u	8.514u	6.844u	7.479u	8.118u	7.643u	8.233u	8.733u	