



INTERNATIONAL INSTITUTE OF
INFORMATION TECHNOLOGY

HYDERABAD

Physically Unclonable Functions

—

Srihari Padmanabhan, Aikya Oruganti

11th November, 2025

11th December, 2025

The Idea



- Leverage the variations in transistors configured as PMOS current mirrors to generate distinct currents
 - Regenerate V_{ref} using diode-connected NMOS
 - Choose a V_{ref} for the next stage based on the challenge bit
 - Implement two parallel chains, each consisting of 32 cascaded stages
 - Compare the voltages to generate a response bit
-

Why it works


- Current mirrors are highly sensitive to threshold voltage and mobility variations from manufacturing, giving excellent device-to-device uniqueness.
- Nonlinear analog current behavior and the amplification of minor mismatches across stages result in high entropy and randomness in response bits.
- The inherent analog nonlinearity in current mirrors makes modeling attacks (such as machine learning) several times harder than for conventional (digital) strong PUFs, giving it a significant security edge.

The circuit

  
- M0: acts as a reference NMOS, drawing some current I set by V_{ref}
- M1, M2, M5: current mirrors, I is replicated in the next two arms
- M3, M4: diode connected NMOS, Regenerate V_{ref} corresponding to the current flowing through that arm
- M6, M7: pass the drain voltage of M3 if the challenge bit is 1
- M8, M9: pass the drain voltage of M4 if the challenge bit is 0




Schematic- Single Stage

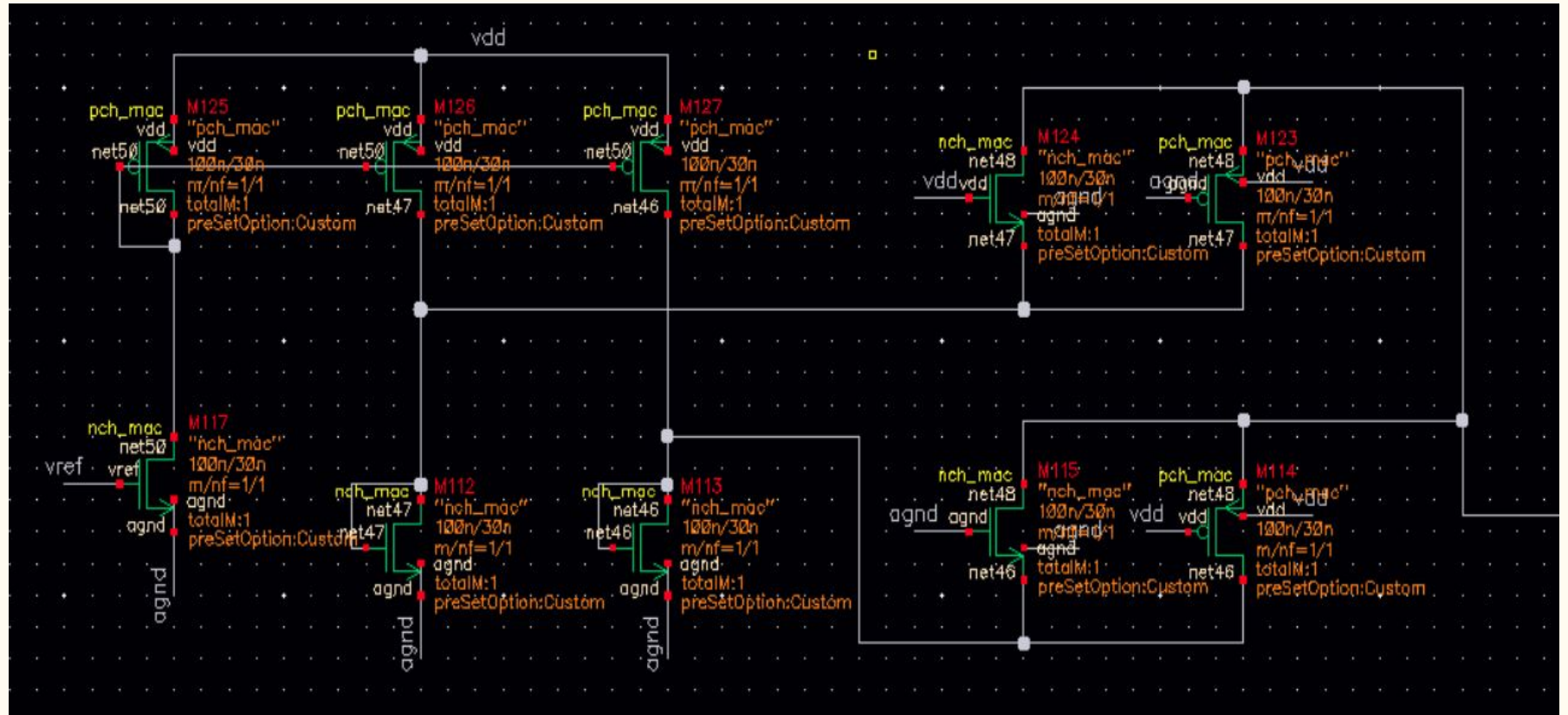

Setup for a 4-bit challenge

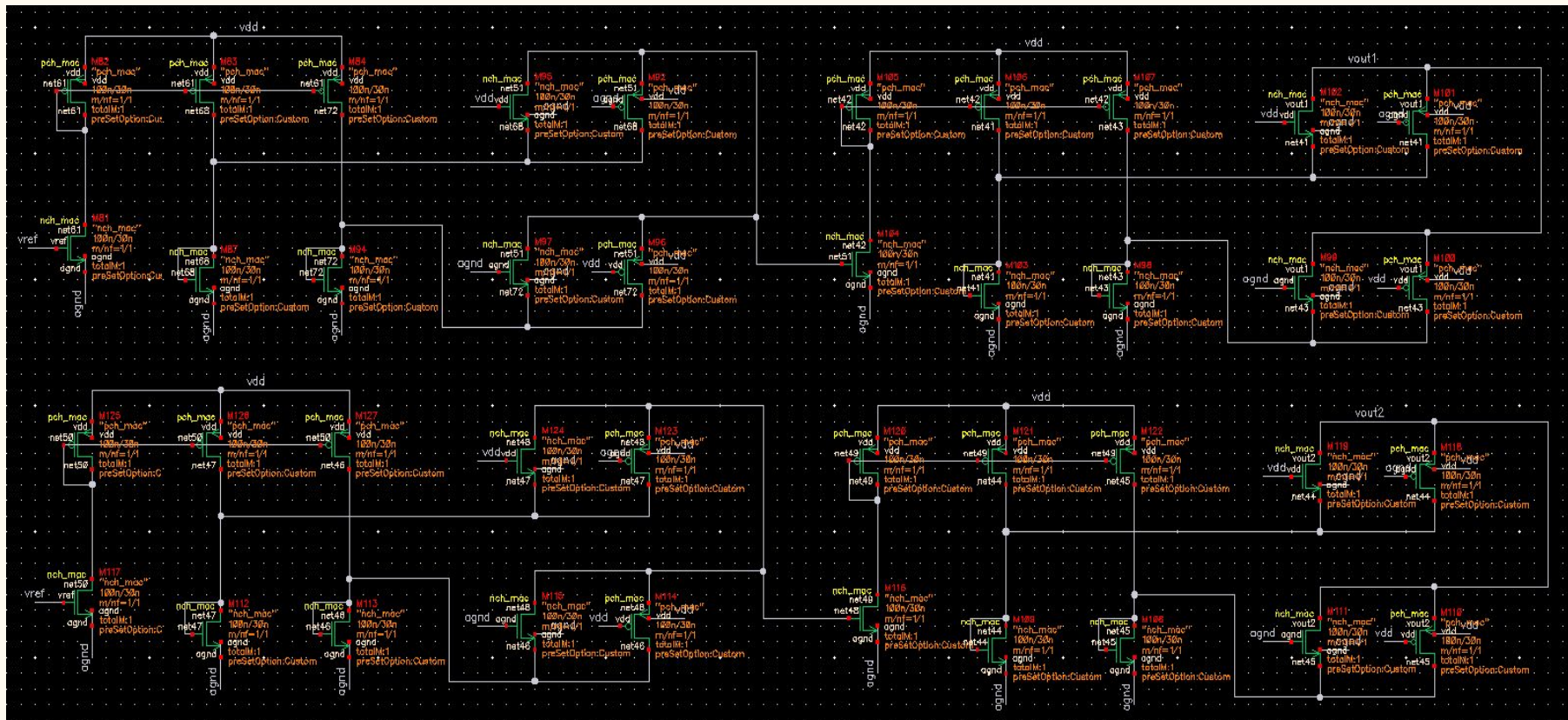

Monte Carlo

Test	Name	Yield	Min	Target	Max	Mean	Std Dev	Cpk	Errors
Yield Estimate: 100 %(100 passed/100 pts) Confidence Level: <not set> Filter: <not set>									
-	 tgate_dc								
	vout1	100% (100/1...	774.4m	info	946.4m	885m	25.34m		0
	vout2	100% (100/1...	796.5m	info	955.8m	885.2m	28.94m		0
	diff	100% (100/1...	-106.9m	info	106.1m	135.8u	39.45m		0


vout1, vout2: Outputs of the two chains

diff= vout1-vout2

response=1 if $\text{diff} > 0$, 0 otherwise

diff


1

 


Results

- The histogram illustrates the distribution of the difference in output voltages of the two chains.
- The distribution adheres approximately to a Gaussian profile, confirming non-ideal, yet symmetric (low skewness), process variability across the chains.
- The mean (135.82μ) is close to zero, supporting unbiased response bit extraction.
- A moderate standard deviation ($\sim 39 \text{ mV}$) ensures sufficient response dispersion, enabling strong inter-device uniqueness.
- Low Kurtosis (peak sharpness) helps bit mapping stability.
- The values are concentrated around the mean indicating high entropy.

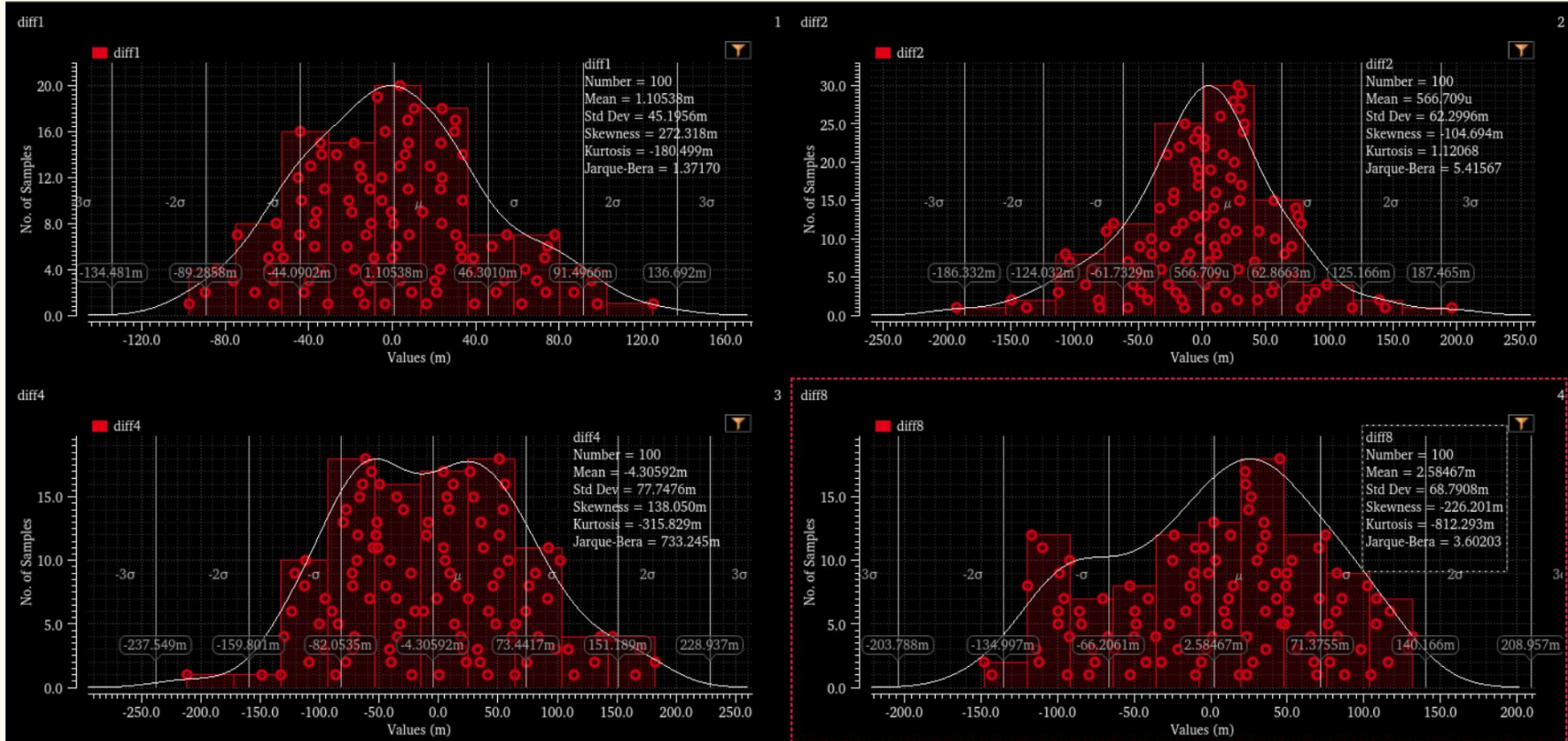Some more results (Varying number of stages)



Combined Histogram

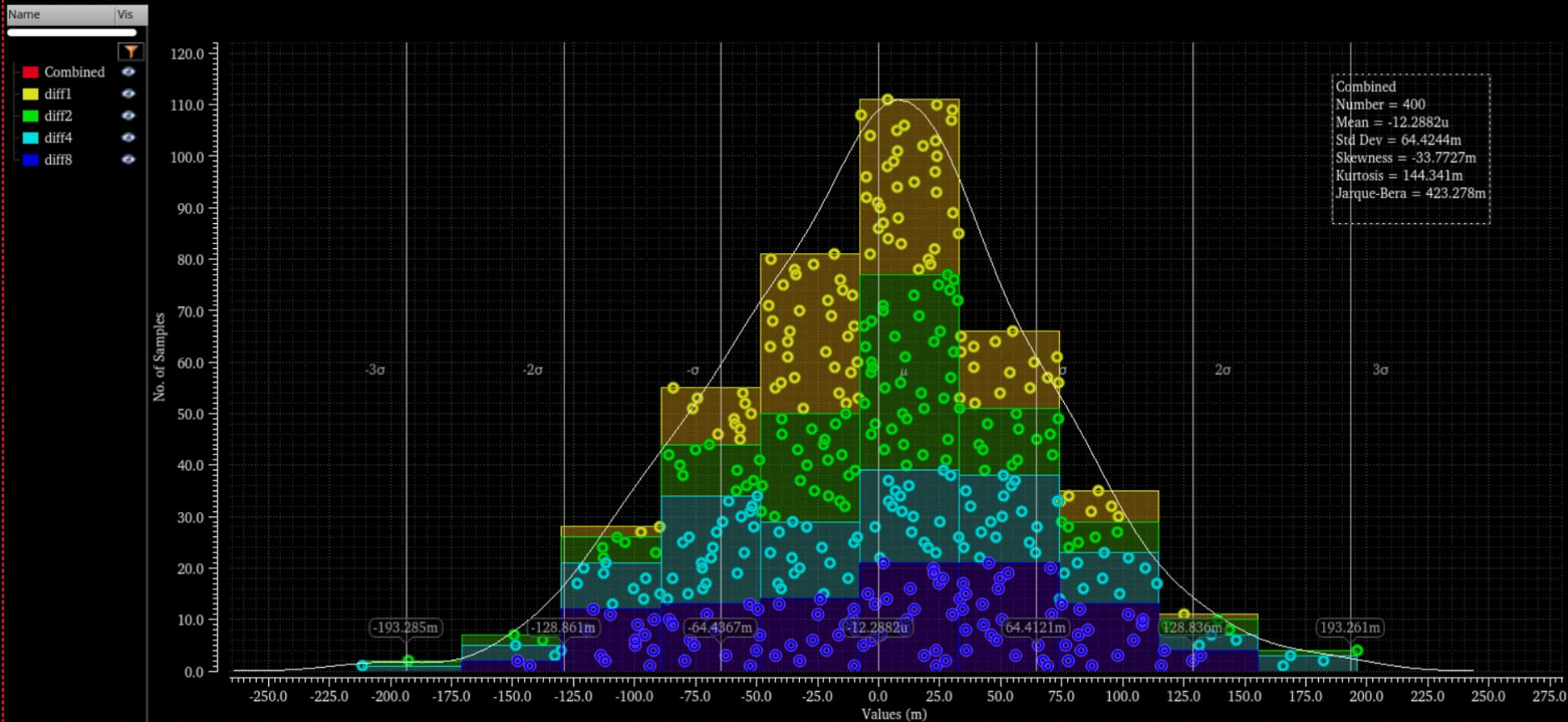

Test Setup

- 8 bit challenge per PUF
- 256 total challenges - output response of 256 bits
- 30 chips (iterations of Monte Carlo mismatch)

Challenges Faced:

- Limited number of Monte Carlo simulations can be run (num chips * num bits in response $< 10k$). Cannot replicate research paper test setup eg 25 chips, 10k challenges. (High compute + RAM requirement)
-

Results

- Uniqueness: 0.495
 - Reliability: 0.992
 - Uniformity: 0.523
 - Bit aliasing: 0.523
-

Uniqueness

Overall uniqueness: Averaged Hamming distance between 256 length outputs over all pairs of chips. Ideal value is 50%.

```
def challenge_wise_uniqueness(all_bits):  
    """  
    For each challenge j, compute mean HD over chip pairs (column-wise).  
    Returns:  
    | ch_uniq: shape (n_challenges,)   
    """  
  
    n_chips, n_ch = all_bits.shape  
    ch_uniq = np.zeros(n_ch)  
    for j in range(n_ch):  
        col = all_bits[:, j]          # (n_chips,)   
        pair_hd = []  
        for i in range(n_chips - 1):  
            pair_hd.append(col[i] ^ col[i+1:]) # xor vs later chips  
        ch_uniq[j] = np.mean(np.concatenate(pair_hd))  
    return ch_uniq
```

References [1] G. C. Gisha, A. S. Chakraborty, R. S. Chakraborty, B. A. Jose, and J. Mathew, “Diode-Triode Current Mirror Inverter PUF: A Novel Mixed-Signal Low Power Analog PUF,” in *Proc. IEEE Int. Midwest Symp. Circuits Syst. (MWSCAS)*, 2023, doi: 10.1109/MWSCAS57524.2023.10405902.


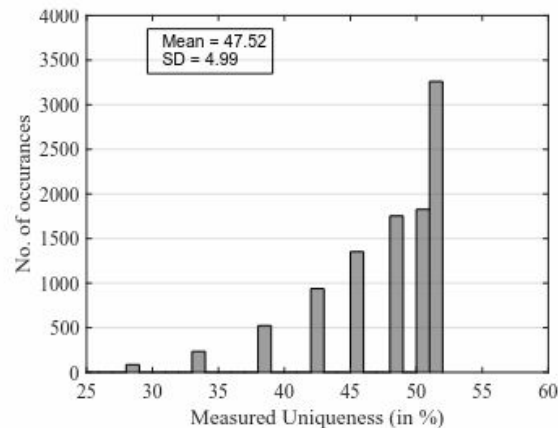
 


Fig. 5. Measured uniqueness distribution.

Reliability

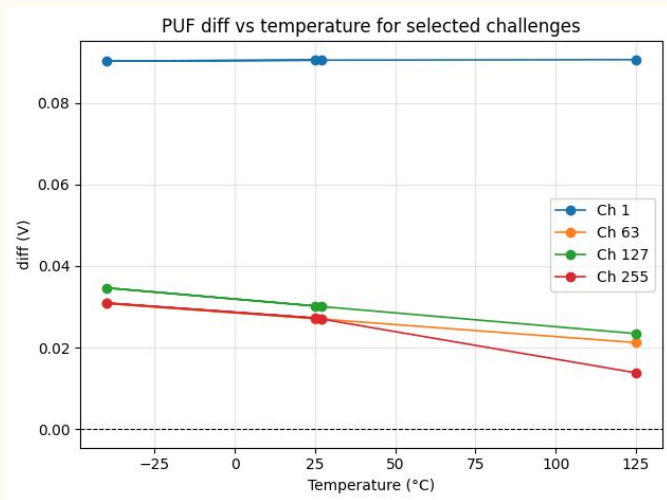
Reliability measures the rate at which a particular PUF generates the same bit string. Ideal value is 100 %.



```
def reliability_from_diffs(diff_temps):  
    """  
    diff_temps : (N, 4) [nominal, -40, 25, 125]  
  
    Returns:  
        rel_per_ch : (N,) reliability per challenge  
        rel_mean   : scalar mean reliability  
        rel_std    : scalar std of reliability  
    """  
  
    # bits at all temps  
    bits_all = (diff_temps > 0).astype(int)      # (N, 4)  
    bits_ref = bits_all[:, 0][:, None]           # (N, 1), nominal as reference  
  
    same = (bits_all == bits_ref).astype(int)     # 1 if matches nominal  
    same_env = same[:, 1:]                       # (N, 3) for T1,T2,T3 only  
  
    rel_per_ch = same_env.mean(axis=1)            # reliability per challenge  
    rel_mean   = rel_per_ch.mean()               # average reliability  
    rel_std    = rel_per_ch.std()                # spread of reliability  
  
    return rel_per_ch, rel_mean, rel_std
```

Uniformity

 
Uniformity measures the degree of variation of the responses of a single PUF chip across different challenges (here over 256 challenges). For maximum random behaviour the average uniformity should be 50%.



```
uniformities = []  
  
for i in range(n_chips):  
    uniformity = bits[i].mean()  
    uniformities.append(uniformity)  
  
uniformities = np.array(uniformities) # shape (n_chips,)
```

Bit aliasing

 Bit aliasing measures the degree of variation in responses of different PUF chips to the same challenge. The ideal value is 50% (Half the PUFs produce a 1, and half 0)



```
def bit_aliasing(all_bits):  
    return all_bits.mean(axis=0)
```